

Ho Chi Minh City National University
University of Information Technology
Computer Engineering



Report
Digital Logic Design
Subject: Encoding B (Prioritized adjacency)
Class: CE118.P11.2

Instructor:

Ta Tri Duc

Performed by students:

Nguyen Ngoc Tho - 23521321

Ho Chi Minh City, 03/2024

Table of contents:	Page
1. Truth table	3
2. Schematic	5
3. Waveform	5

Truth table:

- Next state:

Present State	NEXT STATE		
	CD = 0X	CD = 10	CD = 11
S_0	$S_0/0$	$S_1/0$	$S_2/1$
S_1	$S_1/0$	$S_2/0$	$S_0/0$
S_2	$S_2/0$	$S_0/1$	$S_1/0$

STATE	ENCODING B Q_1Q_0
S_0	0 1
S_1	0 0
S_2	1 0

Next-state map

		CD			
		Q_1Q_0	00	01	11
00		00	00	01	10
01		01	01	10	00
11		XX	XX	XX	XX
10		10	10	00	01
		$Q_1(\text{next}), Q_0(\text{next})$			

$$Q_0(\text{next}) = Q_0C' + Q_1CD' + Q_1'Q_0'CD$$

$$Q_1(\text{next}) = Q_1C' + Q_0CD + Q_1'Q_0'C'D'$$

- JK flipflop: Based on the nextstate-map and truth table of JK flip flop, we draw the truth table of J_0, K_0, J_1, K_1 . From there form the expression to draw the circuit.

Q	$Q(\text{next})$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

J_0

$Q_1 Q_0 \backslash CD$	00	01	11	10
00	0	0	1	0
01	x	x	x	x
11	x	x	x	x
10	0	0	0	1

$$J_0 = Q_1'CD + Q_1CD'$$

K_0

$Q_1 Q_0 \backslash CD$	00	01	11	10
00	x	x	x	x
01	0	0	1	1
11	x	x	x	x
10	x	x	x	x

$$K_0 = C$$

J_1

$Q_1 Q_0 \backslash CD$	00	01	11	10
00	0	0	0	1
01	0	0	1	0
11	x	x	x	x
10	x	x	x	x

$$J_1 = Q_0CD + Q_0'CD'$$

K_1

$Q_1 Q_0 \backslash CD$	00	01	11	10
00	x	x	x	x
01	x	x	x	x
11	x	x	x	x
10	0	0	1	1


$$K_1 = C$$

- Output:


$Q_1 Q_0 \backslash CD$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	0	0	0	1

$$Y = Q_0CD + Q_1CD'$$

Schematic:

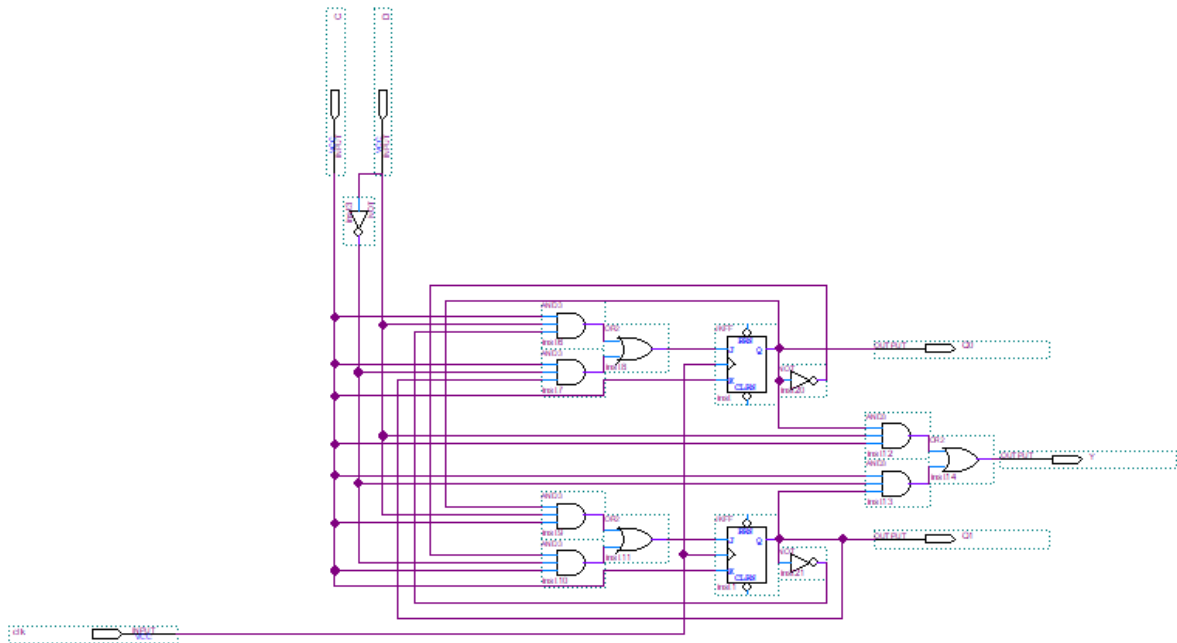

Waveform:

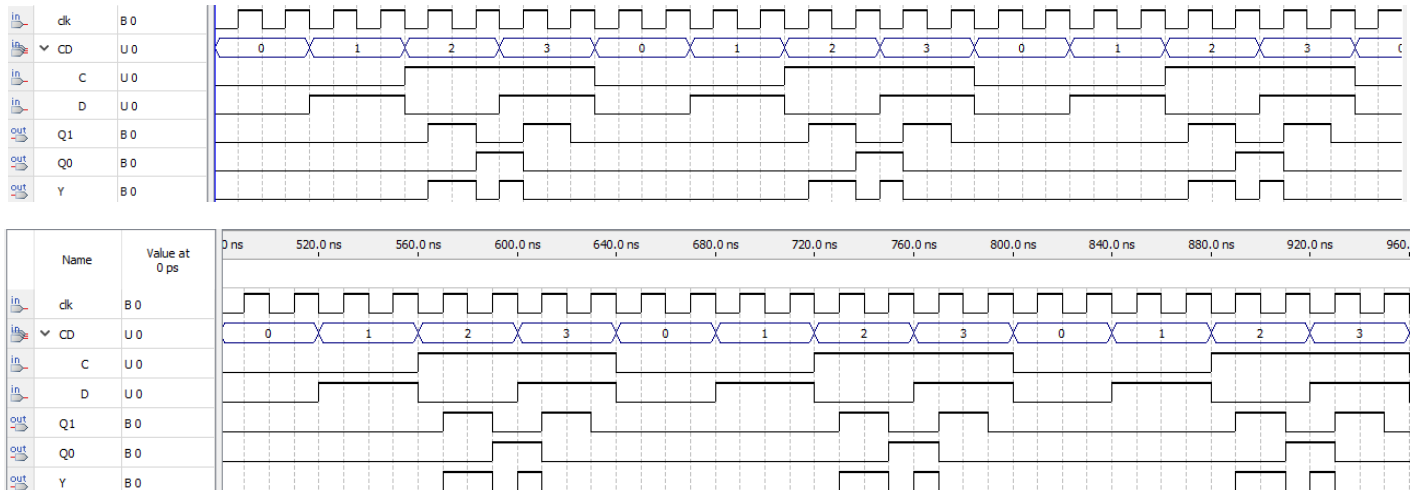

Next-state map

Q ₁ Q ₀	CD			
	00	01	11	10
00	00	00	01	10
01	01	01	10	00
11	X	X	X	X
10	10	10	00	01

Q₁(next), Q₀(next)

$$Q_0(\text{next}) = Q_0C' + Q_1CD' + Q_1'Q_0'CD$$

$$Q_1(\text{next}) = Q_1C' + Q_0CD + Q_1'Q_0'C'D'$$

Based on these 2 tables to check the result of waveform

Q ₁ Q ₀	CD			
	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	0	0	0	1

Y

$$Y = Q_0CD + Q_1CD'$$